

BIRLA INSTITUTE OF TECHNOLOGY, MESRA, RANCHI  
(END SEMESTER EXAMINATION)

CLASS: MTECH  
BRANCH: EEE

SEMESTER : III  
SESSION : MO/19

SUBJECT: EE603 POWER ELECTRONICS SYSTEM DESIGN

TIME: 3 HOURS

FULL MARKS: 50

**INSTRUCTIONS:**

1. The question paper contains 5 questions each of 10 marks and total 50 marks.
  2. Attempt all questions.
  3. The missing data, if any, may be assumed suitably.
  4. Before attempting the question paper, be sure that you have got the correct question paper.
  5. Tables/Data hand book/Graph paper etc. to be supplied to the candidates in the examination hall.
- 

- Q.1(a) Define volt-second balance law. Explain with proper waveforms and mathematical expression of the law for design of an inductor in case of an SMPS. [5]
- Q.1(b) Derive the expression for Inductor (L) for a Buck-Converter feeding a resistive load (R) such that per unit ripple current  $\Delta I/I_0 \ll 1$  where  $I_0$  is average output current. Consider switching period of ' $T_s$ ' seconds and duty cycle of ' $D$ '. [5]
- Q.2(a) Compute area product, number of turns, cross section of wire, and air gap for design of an E-Core inductor of  $20\mu\text{H}$  capable of conducting 5Amp average DC current. Assume maximum flux density of the core to be 0.2 Tesla, current density of wire to be  $3\text{Amp}/\text{mm}^2$ , permeability of the air-gap to be  $4\pi \times 10^{-7} \text{H}/\text{m}$ . [5]
- Q.2(b) Derive relationship between input and output voltage of a Boost Converter for Discontinuous Conduction Mode. [5]
- Q.3(a) Apply concepts of basic DC-DC converters to design a topology for non-isolated bidirectional DC-DC converter. Explain its operation in bidirectional power flow. [5]
- Q.3(b) Draw a power circuit for bidirectional DC-DC converter with isolation between input and output side. Explain its operation in bidirectional power flow. [5]
- Q.4(a) Draw a voltage waveform, load current waveform and firing pulses for a three phase controlled rectifier, with firing angle of  $\frac{\pi}{6}$  Rad. [5]
- Q.4(b) Evaluate harmonic contents present in output voltage of a three phase controlled rectifier under continuous load current. [5]
- Q.5(a) Design a closed loop control of three phase inverter using block diagram in order to maintain a desired output RMS voltage and desired line frequency. Explain its operation. [5]
- Q.5(b) Design an analogue electrical circuit in order to explain heat dissipation in power semiconductor devices. [5]

:::::25/11/2019:::::M