

**BIRLA INSTITUTE OF TECHNOLOGY, MESRA, RANCHI
(END SEMESTER EXAMINATION)**

CLASS: BTECH
BRANCH: CS/AI&ML/ECE/EEE

SEMESTER : I
SESSION : MO/2022

SUBJECT: EC101 BASICS OF ELECTRONICS AND COMMUNICATION ENGG.
TIME: 3 Hours

FULL MARKS: 50

INSTRUCTIONS:

1. The question paper contains 5 questions each of 10 marks and total 50 marks.
2. Attempt all questions.
3. The missing data, if any, may be assumed suitably.
4. Before attempting the question paper, be sure that you have got the correct question paper.
5. Tables/Data hand book/Graph paper etc. to be supplied to the candidates in the examination hall.

- | | | | |
|--|-----|-----|-----|
| Q.1(a) Explain the V - I Characteristics curve of Zener Diode. Compare the avalanche breakdown mechanism with the Zener breakdown mechanism for a Zener Diode. | [5] | CO | BL |
| | | CO1 | BL2 |
| Q.1(b) With neat sketch, explain the working principle of a full wave center tapped type rectifier with a capacitor filter. State the formula for ripple factor of a capacitive filter. | [5] | CO1 | BL2 |
| Q.2(a) Draw the input and output characteristics of common-emitter configuration of NPN transistor. Derive the relation between α , β and γ . Deduce the dc bias voltage V_{CE} and the current I_C for voltage divider configuration shown in figure 1. | [5] | CO2 | BL4 |

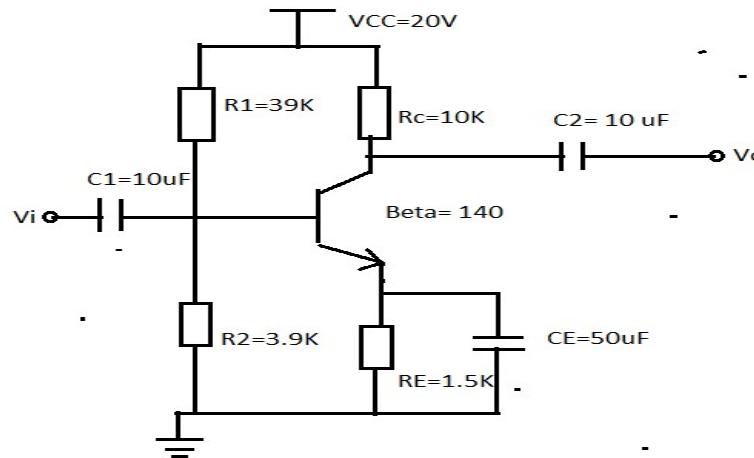


FIGURE 1

- | | | | |
|--|-----|-----|-----|
| Q.2(b) Derive the Shockley's equation for drain current for JFET and show the Pinch off Region (V_p) in a JFET Characteristics curve. | [5] | CO2 | BL2 |
| Q.3(a) Explain the working of the RC phase shift oscillator. Derive its frequency of oscillation. | [5] | CO2 | BL2 |
| Q.3(b) In the circuit shown in figure 2, $R_1 = 100$ K Ohm, $R_2 = 150$ K Ohm and $R_f = 300$ K Ohm. If $V_1 = 1$ V and the op-amp saturates at ± 15 V then examine the range of V_2 for linear operation. | [5] | CO3 | BL4 |

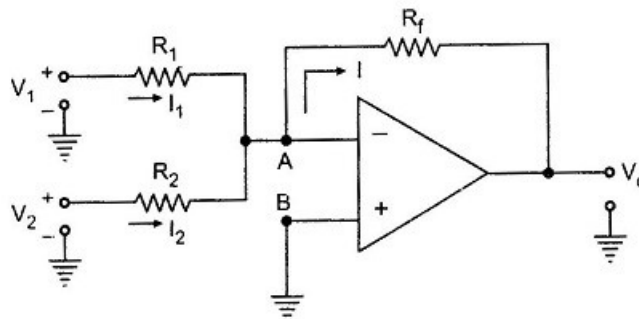


Fig. 2.25 Inverting summer

FIGURE 2

PTO

- Q.4(a) Explain Half adder, full adder circuits. How an XOR gate can be used as selective inverter? [5] CO4 BL2
- Q.4(b) Design a 4-bit adder/subtractor circuit using full adders and X-OR gates as selective inverter. [5] CO4 BL5
- Q.5(a) Explain amplitude modulation. Derive the relationship between total transmitted power and carrier power of AM signal. Calculate its transmission power efficiency. [5] CO5 BL2
- Q.5(b) An AM signal has a peak unmodulated carrier voltage, $V_c = 100$ V, a load resistance, $R_L = 50 \Omega$, and a modulation index, $m_a = 1$. Determine the carrier power, total sideband power, and total power of the modulated AM signal. Also sketch the AM power spectrum. [5] CO5 BL4

.....20/03/2023.....M