

**BIRLA INSTITUTE OF TECHNOLOGY, MESRA, RANCHI  
(END SEMESTER EXAMINATION)**

CLASS: BTECH  
BRANCH: ECE

SEMESTER : V  
SESSION : MO/2022

SUBJECT: EC319 VLSI SYSTEMS



TIME: 3:00 Hours

FULL MARKS: 50

**INSTRUCTIONS:**

1. The question paper contains 5 questions each of 10 marks and total 50 marks.
  2. Attempt all questions.
  3. The missing data, if any, may be assumed suitably.
  4. Before attempting the question paper, be sure that you have got the correct question paper.
  5. Tables/Data hand book/Graph paper etc. to be supplied to the candidates in the examination hall.
- 


- |   |     |         |         |
|---|-----|---------|---------|
| Q1 (a) Find the region of operation of the pMOSFET and nMOSFET shown below. | [2] | CO<br>1 | BL<br>2 |
|---|-----|---------|---------|

  

- |  |     |   |   |
|--|-----|---|---|
| Q1 (b) List various secondary effects in a short-channel MOSFETs?  | [3] | 1 | 1 |
| Q1 (c) Write the expression of dynamic power consumption. Explain each term in it. Write the expression of Power-Delay Product (PDP) and Energy-Delay Product (EDP). Explain each term in them.            | [5] | 1 | 3 |
| Q2 (a) A wire, which is 10 cm long and 1 μm wide, is routed on the polycide, the sheet resistance of which is 4 Ohm-per-square. Compute the total resistance of the wire.                                  | [2] | 2 | 3 |
| Q2 (b) What is skin effect and skin depth? Express the equation of skin depth mentioning each term in minimum words.   | [3] | 2 | 2 |
| Q2 (c) Explain how a Schmitt trigger circuit can guard against noise-induced false switching when used in an input pad. Substantiate your answer with suitable diagram.                                    | [5] | 2 | 3 |
| Q3 (a) Explain why pseudo nMOS logic circuits are called ratioed circuits?   | [2] | 3 | 4 |
| Q3 (b) Diagram the transistor-level circuit diagram of an inverter and implement the same with Verilog HDL using switch-level modeling style.  | [3] | 3 | 4 |
| Q3 (c) Using CMOS logic styles realize the Co (carry out) function, which is given by $Co = A.B + Ci.(A+B)$ , and SUM function, which is given by $SUM = A.B.Ci + (A+B.Ci)$ , where Ci is the input carry. | [5] | 3 | 4 |
| Q4 (a) Schematize transistor-level circuit of CMOS positive-level-sensitive D latch with minimum number MOSFET.  | [2] | 4 | 5 |
| Q4 (b) Schematize transistor-level implementation of SR flip-flop with NAND as well as NOR gate.   | [3] | 4 | 5 |
| Q4 (c) Schematize multiplexer-based NMOS latch using NMOS-only pass transistors. Explain its advantages and disadvantages with proper reasoning.   | [5] | 4 | 5 |

PTO

 - Q5 (a) A MOSFET is biased at a drain current of 0.5 mA. If  $\mu_n C_{ox} = 100 \mu\text{A}/\text{V}^2$ ,  $W/L = 10$ , and  $\lambda = 0.1\text{V}^{-1}$ , estimate its small-signal parameter  $g_m$ . [2] 5 5
- Q5 (b) Estimate the small-signal voltage gain of the CS stage shown in Fig. 7.6 if  $I_D = 1\text{ mA}$ ,  $\mu_n C_{ox} = 100 \mu\text{A}/\text{V}^2$ ,  $V_{TH} = 0.5\text{ V}$ , and  $\lambda = 0$ . Verify that  $M_1$  operates in saturation. [3] 5 5



- Q5 (c) Schematize CS stage with load resistor  $R_D$  and source degeneration resistor  $R_S$ . Schematize its small signal model and derive the expression of its voltage gain. [5] 5 6

:::::28/11/2022:::::M