

**BIRLA INSTITUTE OF TECHNOLOGY, MESRA, RANCHI  
(END SEMESTER EXAMINATION MO/2022)**

CLASS: BTECH  
BRANCH: ECE

SEMESTER : V  
SESSION:MO-2022

SUBJECT: EC325 R1DIGITAL SYSTEMS DESIGN WITH FPGAS


TIME: 03 Hours

FULL MARKS: 50


**INSTRUCTIONS:**

1. The question paper contains 5 questions each of 10 marks and total 50 marks.
2. Attempt all questions.
3. The missing data, if any, may be assumed suitably.
4. Tables/Data handbook/Graph paper etc., if applicable, will be supplied to the candidates

 - Q.1(a) Why not incorporate programmable or adaptable components into all structures? [2]  
 Q.1(b) What are some of the most essential goals of the design's standard-cell placement and routing tools? [3]  
 Q.1(c) What are the different FPGA methodologies? Explain the same with neat diagram. [5]
- Q.2 (a) Where do skew and jitter come from? [2]  
 Q.2 (b) Write a VHDL Code for 2 to 4 decoder using if else statement? [3]  
 Q.2(c) Design a XNOR gate with Verilog code using behavioral modeling? [5]
- Q.3 (a) Mention a couple of the adder's optimization schemes? [2]  
 Q.3 (b) What are data paths in digital processor architectures? [3]  
 Q.3(c) Design a transmission gate adder circuit and explain its features. [5]
- Q.4(a) Outline the several types of memory. [2]  
 Q.4(b) Implement and demonstrate the operation of the MOS cell's NOR ROM. [3]  
 Q.4(c) Evaluate the propagation delay associated with NOR ROM. Resistance/cell: 35ohm and 0.15ohm, wire capacitance/cell: 0.65 fF and 0.83 fF, and gate capacitance/cell: 5.10 fF and 2.60 fF, respectively for word and bit line. [5]



 - Q.5(a) Define the term d-frontiers and j-frontiers? [2]  
 Q.5(b) Determine the output Y for a stuck-at-fault at P=0. [3]



- Q.5(c) Give the different classifications of open circuit faults and briefly explain them. [5]