

**BIRLA INSTITUTE OF TECHNOLOGY, MESRA, RANCHI
(MID SEMESTER EXAMINATION)**

**CLASS: BTECH
BRANCH: EEE**

**SEMESTER: V
SESSION: MO/2022**

SUBJECT: EE357 ELECTRONIC DEVICES AND ANALOG CIRCUITS

TIME: 2 HOURS


FULL MARKS: 25

INSTRUCTIONS:

1. The total marks of the questions are 25.
 2. Candidates attempt for all 25 marks.
 3. Before attempting the question paper, be sure that you have got the correct question paper.
 4. The missing data, if any, may be assumed suitably.
 5. Tables/Data hand book/Graph paper etc. to be supplied to the candidates in the examination hall.
-

- | | | | |
|----|--|-------------|----|
| | | CO | BL |
| Q1 | (a) What is diffusion capacitance? | [2] CO1,CO2 | L1 |
| Q1 | (b) Prove that transition capacitance $C_T = \epsilon A/W$ | [3] CO1,CO2 | L2 |

- | | | | |
|----|--|-------------|----|
| | | CO | BL |
| Q2 | (a) Find out the ripple factor of half wave rectifier. | [2] CO1,CO2 | L2 |
| Q2 | (b) | [3] CO1,CO2 | L3 |

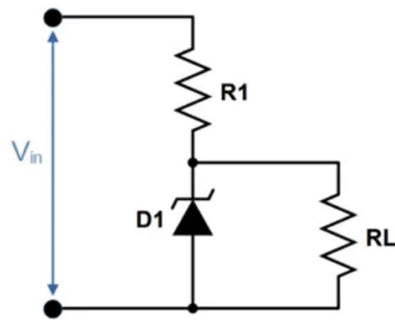

Given that: $R_1=220 \text{ ohm}$, $V_Z=20V$,
 $I_{ZM}=60mA$, $R_L=1.2k\text{ohm}$, Find the range of V_{in} .

- | | | | |
|----|---|-------------|----|
| | | CO | BL |
| Q3 | (a) What are the advantages and disadvantages of LED. | [2] CO1,CO2 | L2 |
| Q3 | (b) In a half wave rectifier diode resistance= 10 ohm load resistance= 100ohm, secondary of transformer supply 50V(rms). Find (a) the peak current (b) the total input ac power (c) the DC voltage. | [3] CO1,CO2 | L3 |
| | | | |
| Q4 | (a) What are the different modes of BJT. | [2] CO1,CO2 | L2 |
| Q4 | (b) Draw the input and output characteristics of CE configuration, also explain in brief. | [3] CO1,CO2 | L2 |
| | | | |
| Q5 | (a) Draw the transconductance curve of a JFET, also write the current equation I_d . | [2] CO1,CO2 | L2 |
| Q5 | (b) What is IGBT? Explain its characteristics. | [3] CO1,CO2 | L2 |