

BIRLA INSTITUTE OF TECHNOLOGY, MESRA, RANCHI
(END SEMESTER EXAMINATION MO-2022)

CLASS: B.TECH
BRANCH: EEE

SEMESTER : VII
SESSION : MO/2022

TIME: 03 HOURS

SUBJECT: EE507 ADVANCED POWER ELECTRONICS

FULL MARKS: 50

INSTRUCTIONS:

1. The question paper contains 5 questions each of 10 marks and total 50 marks.
 2. Attempt all questions.
 3. The missing data, if any, may be assumed suitably.
 4. Tables/Data handbook/Graph paper etc., if applicable, will be supplied to the candidates
-

- Q.1(a) Draw static and dynamic characteristics of IGBT. [2]
Q.1(b) Explain the reverse recovery phenomenon of thyristors. [3]
Q.1(c) What are the four types of heat transfer mechanisms? Explain them briefly. [5]
- Q.2(a) What are the categories of isolated converters? [2]
Q.2(b) What are the advantages of the dual switch forward converter and explain its functioning? [3]
Q.2(c) Design full bridge converter topology and discuss the operation of the full-bridge topology. [5]
- Q.3(a) What is the basic concept of multilevel converters? [2]
Q.3(b) What are the advantages of cascaded multilevel inverters? [3]
Q.3(c) Design the flying capacitor multilevel inverter and discuss the operational features. [5]
- Q.4(a) What is the dead zone of a resonant inverter? [2]
Q.4(b) A series resonant inverter with series loaded delivers a power of 1 kW at resonance. The load resistance is $R = 10\text{ohm}$ and resonant frequency is 20 kHz. Determine (a) DC input voltage V_s , (b) quality factor, it is required the load power to 250 w by frequency control so that $u=0.8$ (c) the inductor L and (d) the capacitor C . [3]
Q.4(c) Explain the step by step operational behaviour of a zero voltage switching resonant converter. [5]
- Q.5(a) What are the requirements for industrial gate driver circuit? [2]
Q.5(b) Design industrial gate driver circuit using TLP 250. [3]
Q.5(c) Compare the three basic types of the multilevel inverter topologies. [5]

:::::21/11/2022 M:::::