

**BIRLA INSTITUTE OF TECHNOLOGY, MESRA, RANCHI**  
(MID SEMESTER EXAMINATION MO/2023)

CLASS: B.TECH/IMSC.  
BRANCH: BT/CIVIL/CHEMICAL/MECH/PIE/FT/PHYSICS

SEMESTER : I  
SESSION : MO/2023

SUBJECT: EE101 BASIC OF ELECTRICAL ENGINEERING


TIME: 02 Hours

FULL MARKS: 25


**INSTRUCTIONS:**

1. The question paper contains 5 questions each of 5 marks and total 25 marks.
2. Attempt all questions.
3. The missing data, if any, may be assumed suitably.
4. Tables/Data handbook/Graph paper etc., if applicable, will be supplied to the candidates


- |  |     |     |     |
|--|-----|-----|-----|
| Q.1(a) Define (i) bilateral and unilateral elements (ii) active and passive elements.  | [2] | CO  | BL  |
| Q.1(b) Apply mesh analysis to calculate the current through the $3\Omega$ resistor and the voltage $V_x$ of the given circuit. | [3] | CO1 | BL1 |

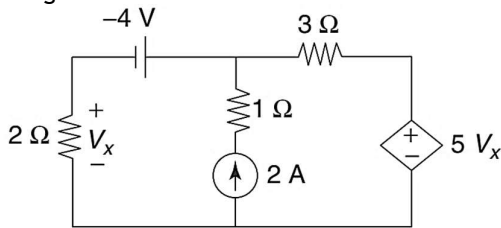


- |  |     |     |     |
|--|-----|-----|-----|
| Q.2(a) Apply KVL/KCL to calculate the value of $i_x$ and $v$ in the given circuit. | [2] | CO1 | BL3 |
|--|-----|-----|-----|

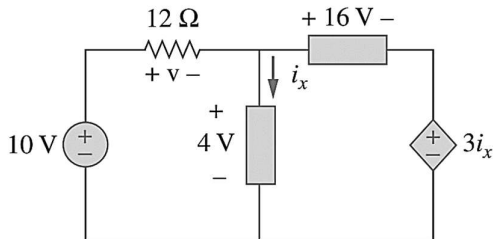

- |   |     |     |     |
|---|-----|-----|-----|
| Q.2(b) Apply star delta conversion, to estimate the equivalent resistance $R_{ab}$ across the terminals a-b and the current $i$ in the circuit below. | [3] | CO1 | BL3 |
|---|-----|-----|-----|

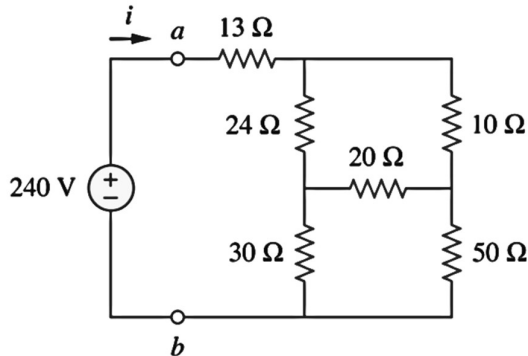

- |  |     |     |     |
|--|-----|-----|-----|
| Q.3(a) For the circuit given below, calculate the current, voltage and power associated with the $20k\Omega$ resistor. | [2] | CO1 | BL3 |
|--|-----|-----|-----|

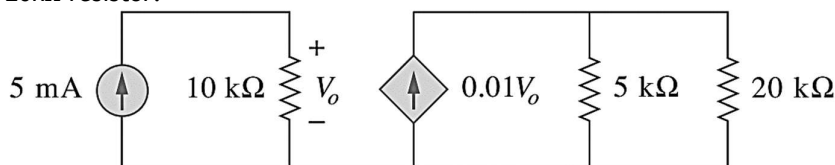


- |   |     |     |     |
|---|-----|-----|-----|
| Q.3(b) Two impedances of $(14 + j5)\Omega$ and $(18 + j10)\Omega$ are connected in parallel across a 200 V, 50 Hz AC supply. Determine (i) the current in each branch and total current, (ii) the power factor of each branch, and (iii) draw the phasor diagram. | [3] | CO2 | BL3 |
|---|-----|-----|-----|

Q.4(a) Define the RMS value and average value of a signal.

[2] CO2 BL1

Q.4(b) Calculate the RMS and average value of the waveform shown below:

[3] CO2 BL3

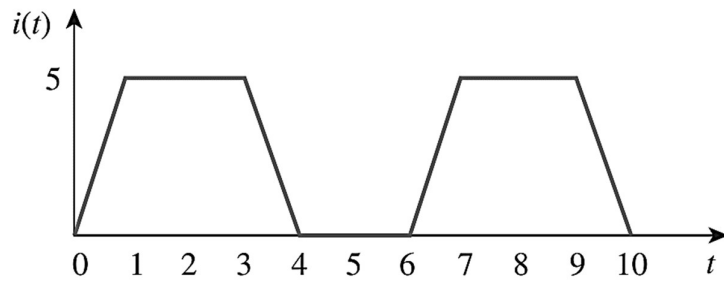

Q.5(a) Define (i) Q-factor and (ii) Bandwidth

[2] CO2 BL1

Q.5(b) A series resonant circuit has an impedance of  $500\ \Omega$  at resonant frequency. Cut-off frequencies are 10 kHz and 100 Hz. Calculate (i) resonant frequency, (ii) value of L, C, and (iii) quality factor at resonant frequency.

[3] CO2 BL3

:::::18/10/2023:::::