

CLASS: B-TECH
BRANCH: ECE

SEMESTER : III/ADD
SESSION : MO/2024

SUBJECT: EC209 NETWORK THEORY

TIME: 02 Hours

FULL MARKS: 25

INSTRUCTIONS:

1. The question paper contains 5 questions each of 5 marks and total 25 marks.
2. Attempt all questions.
3. The missing data, if any, may be assumed suitably.
4. Tables/Data handbook/Graph paper etc., if applicable, will be supplied to the candidates


Q.1(a) A reduced incidence matrix of a graph is given by

CO BL
[2] CO-1 BL-1

$$a = \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 1 \\ 0 & -1 & 1 & -1 & 0 & 0 \\ -1 & 0 & -1 & 0 & -1 & 0 \end{bmatrix}$$

Find out the number of possible trees.

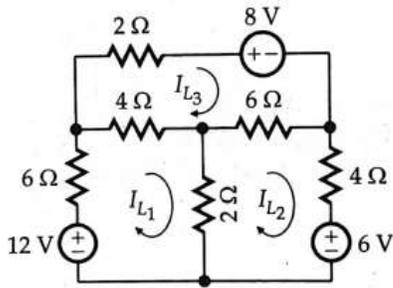Q.1(b) A network is shown in the given figure. Write down the tie-set matrix by [3] CO-1 BL-3 considering a suitable tree.




Q.2(a) (i) Write the relation among reduced incidence matrix $[A]$, branch admittance matrix $[Y_b]$, current source matrix $[I_s]$ and voltage source matrix $[V_s]$ and node voltage $[V_n]$.

[2] CO-1 BL-3


(ii) Write the relation among fundamental cut set matrix $[Q]$, branch admittance matrix $[Y_b]$, twig voltage matrix $[V_T]$, current source matrix $[I_s]$ and voltage source matrix $[V_s]$.

Q.2(b) For the given network in the Figure, draw a graph and select a tree with branches having resistance 3 of ohm (branch-2) and 4 ohm (branch-4, having resistance 4 and voltage source 24 in series). Determine the Tie-set matrix. Using topological form of KVL equation, find various branch currents. The branch numbers are marked with integers and node numbers are encircled.


[3] CO-1 BL-3

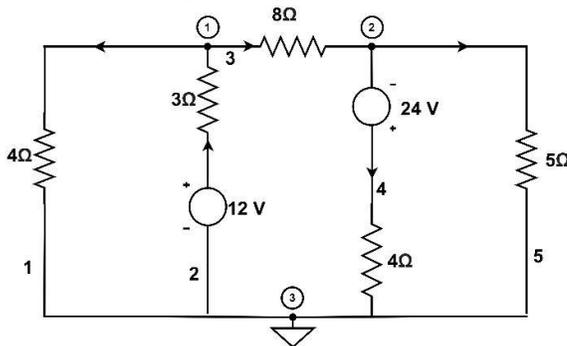

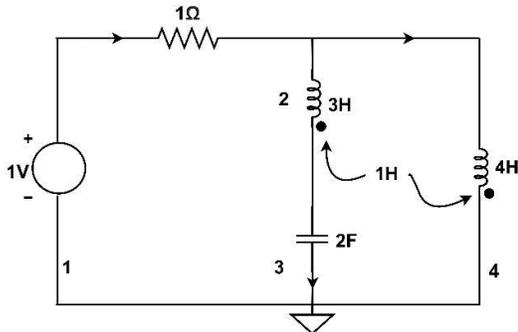
- Q.3(a) Define Tellegen's and substitution theorem. [2] CO-1 BL-1,2
 Q.3(b) For the network shown in the Figure, write down the f-cut set matrix for the tree having 3 H inductor and 2 F capacitor as twigs, and write the network equilibrium equation using Cut-set. [3] CO-1 BL-3,4



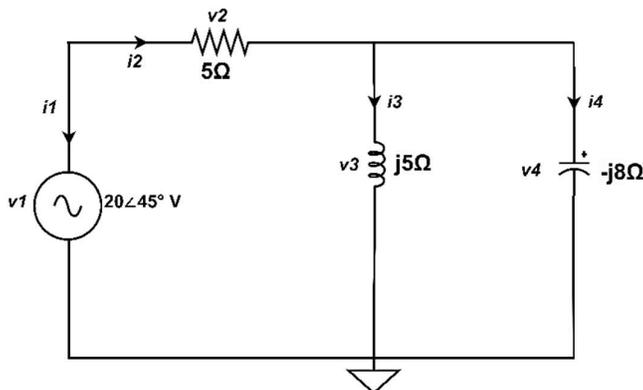- Q.4(a) Verify the Tellegen's theorem for the network shown in the figure. [2] CO-2 BL-1,2



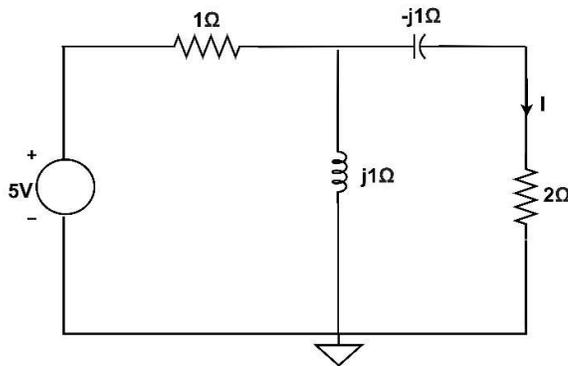- Q.4(b) Verify reciprocity theorem for the network shown in the figure in which voltage source of 5 volt cause a current 'I' in the 2 ohm resistor. Find the value of 'I'. [3] CO-2 BL-1,2



- Q.5(a) Define state and state variable. Form the state equations for the RLC series circuit. [2] CO-2 BL-1,2
 Q.5(b) In the network shown in the figure, verify the substitution theorem by replacing the 6 ohm resistor by a voltage source. [3] CO-2 BL-3

