

BIRLA INSTITUTE OF TECHNOLOGY, MESRA, RANCHI
(MID SEMESTER EXAMINATION MO/2024)

CLASS: B.TECH.
BRANCH: ECE

SEMESTER : VII
SESSION : MO/2024

SUBJECT: EC401R1 MICROWAVE THEORY AND TECHNIQUES


TIME: 02 Hours

FULL MARKS: 25


INSTRUCTIONS:

1. The question paper contains 5 questions each of 5 marks and total 25 marks.
2. Attempt all questions.
3. The missing data, if any, may be assumed suitably.
4. Tables/Data handbook/Graph paper etc., if applicable, will be supplied to the candidates

- | | | | |
|--|-----|------|------|
| Q.1(a) Write about the various advantages and applications of microwave. | [2] | CO I | BL I |
| Q.1(b) Determine the scattering parameters of the 3 dB attenuator circuit shown in Fig. 1(b) | [3] | CO I | BL V |

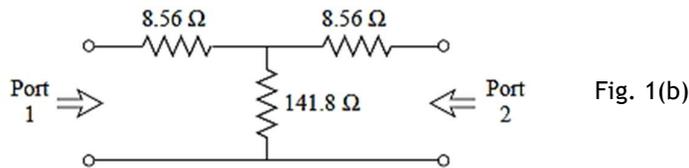

- | | | | |
|---|-----|------|--------|
| Q.2(a) Obtain the relationship between transmission [ABCD]-matrix and [S]-matrix | [2] | CO I | BL II |
| Q.2(b) Obtain the transmission [ABCD] matrix of the two-port network shown in Fig. 2(b) | [3] | CO I | BL III |

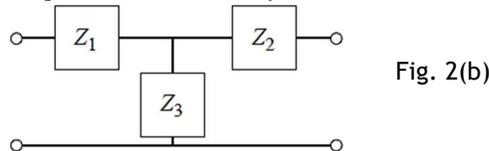

- | | | | |
|--|-----|-------|--------|
| Q.3(a) Derive the expression of [S]-parameters to [Z]-parameters conversion formula. | [2] | CO I | BL II |
| Q.3(b) Using an even and odd mode analysis, determine the [S]-matrix of Wilkinson power divider for equal power division. | [3] | CO II | BL V |
| Q.4(a) Prove that a three-port network can't be lossless, reciprocal and perfectly matched at all the ports simultaneously. | [2] | CO II | BL II |
| Q.4(b) In an H-plane Tee junction, 20 mw power is applied to port 3 that is perfectly matched to the junction. Calculate the power delivered to the load 60 Ω and 75 Ω connected to port 1 and port 2, respectively. | [3] | CO II | BL III |
| Q.5(a) Explain the coupled line theory for the design of coupled line coupler. | [2] | CO II | BL II |
| Q.5(b) A 90-degree symmetric directional coupler has the coupling factor of 8.34 dB. determine the phase and amplitude at ports 2 and 3 relative to port 1. | [3] | CO II | BL V |