

**BIRLA INSTITUTE OF TECHNOLOGY, MESRA, RANCHI
(END SEMESTER EXAMINATION)**

**CLASS: BTECH
BRANCH: EEE**

**SEMESTER : VII
SESSION : MO/2024**

SUBJECT: EE507 ADVANCED POWER ELECTRONICS

TIME: 3 Hours

FULL MARKS: 50

INSTRUCTIONS:

1. The question paper contains 5 questions each of 10 marks and total 50 marks.
 2. Attempt all questions.
 3. The missing data, if any, may be assumed suitably.
 4. Before attempting the question paper, be sure that you have got the correct question paper.
 5. Tables/Data hand book/Graph paper etc. to be supplied to the candidates in the examination hall.
-

		CO	BL
Q.1(a)	Explain the working of the gate driver circuit in IGBT with proper waveforms?	[5] CO1&CO2	BL2
Q.1(b)	Justify the role of totem pole arrangement in a gate driver circuit? How the need of floating supply is established in a gate driver circuit?	[5] CO1&CO2	BL1&B5
Q.2(a)	With proper circuit diagram and waveforms explain the working of an isolated push-pull converter? Identify the short comings of push-pull converter over isolated cuk converter?	[5] CO2&CO3	BL3
Q.2(b)	Compare the working of an isolated forward converter to an isolated flyback converter?	[5] CO3	BL4
Q.3(a)	Illustrate the significance of third harmonic injection in sine PWM? Derive the conditions required for it.	[5] CO3&CO4	BL2
Q.3(b)	Design a single phase asymmetric 9-level CHB converter voltage with two H-bridges at 1:3 ratio of DC link voltage. Examine the switching states and output waveforms for it.	[5] CO4&CO5	BL4& BL6
Q.4(a)	Compare the working of Unipolar and Bipolar PWM switching in a single phase VSI? List different modulation strategies in a PWM.	[5] CO2&CO3	BL4
Q.4(b)	Design a ZCS resonant buck converter and evaluate inductor current, capacitor voltage and switch voltages assuming different modes of operation.	[5] CO4	BL5&BL6
Q.5(a)	Define Resonant Converters? With proper justification explain the conditions of non-overlapping and overlapping waveforms in series resonant inverter with bidirectional switches.	[5] CO2&CO3	BL1&BL3
Q.5(b)	With the help of pin diagram explain the working of UC 3843 ?	[5] CO2	BL3

:::19/11/2024:::M