

**BIRLA INSTITUTE OF TECHNOLOGY, MESRA, RANCHI
(END SEMESTER EXAMINATION)**

**CLASS: M.Tech
BRANCH: Electrical Engineering**

**SEMESTER : I
SESSION : MO/2024**

SUBJECT: EE507 ADVANCED POWER ELECTRONICS


TIME: 3 Hours

FULL MARKS: 50

INSTRUCTIONS:

1. The question paper contains 5 questions each of 10 marks and total 50 marks.
 2. Attempt all questions.
 3. The missing data, if any, may be assumed suitably.
 4. Before attempting the question paper, be sure that you have got the correct question paper.
 5. Tables/Data hand book/Graph paper etc. to be supplied to the candidates in the examination hall.
-

- | | CO | BL |
|--|-------|----|
| Q.1(a) Draw cross-sectional diagram of POWER MOSFET. Draw switching characteristics of Power MOSFET. | [5] 1 | 2 |
| Q.1(b) In the diode and LC network, the capacitor is charged to voltage V_0 with upper plate positive. Switch S is closed at $t=0$. Derive expressions for current through and voltage across C. Assume other data. | [5] 1 | 2 |

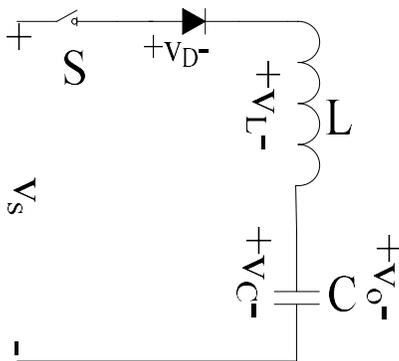

- | | | |
|--|-------|---|
| Q.2(a) With the help of equivalent circuit diagram illustrate operating principle of Half bridge converter along with the theoretical waveforms with relevant equations | [5] 2 | 3 |
| Q.2(b) Illustrate the operation of the forward converter with demagnetizing winding of 100W. Assume other specifications. | [5] 2 | 3 |
| Q.3(a) Examine the operating principle of cascaded multilevel converter with a neat circuit diagram and relate with other multilevel inverters | [5] 3 | 4 |
| Q.3(b) Analyse multiple pulse width modulation technique and compare with sinusoidal PWM technique | [5] 3 | 4 |
| Q.4(a) Evaluate the Zero Voltage Switching Resonant Converter with the theoretical waveforms of Capacitor voltage and inductor current, derive the resonant capacitor voltage during resonant state. | [5] 4 | 5 |
| Q.4(b) Derive the relation of current through resonant inductor during mode 2 and mode 3 i.e., during resonant state. | [5] 4 | 5 |
| Q.5(a) Design a IGBT gate drive circuit | [5] 5 | 6 |
| Q.5(b) Devise an intelligent power module control strategy for an inverter | [5] 5 | 6 |

:::::21/11/2024 E:::::