

**BIRLA INSTITUTE OF TECHNOLOGY, MESRA, RANCHI
(MID SEMESTER EXAMINATION)**

**CLASS: BTECH
BRANCH: ECE/EEE/CSE/AIML**

**SEMESTER : I
SESSION : MO/2025**

SUBJECT: EC24101 BASIC ELECTRONICS


TIME: 02 Hours

FULL MARKS: 25

INSTRUCTIONS:

1. The question paper contains 5 questions each of 5 marks and total 25 marks.
 2. Attempt all questions.
 3. The missing data, if any, may be assumed suitably.
 4. Tables/Data handbook/Graph paper etc., if applicable, will be supplied to the candidates
-

		CO	BL
Q.1(a) Using your understanding of semiconductor behavior, explain how VI characteristics of a silicon diode change when the temperature increases from 25°C-75°C.	[2]	1	3
Q.1(b) Explain the construction and working of a PN junction diode and describe how depletion region is formed with neatly labeled energy band diagram.	[3]	1	2
Q.2(a) A germanium diode carries a current of 1mA at room temperature when a forward bias of 0.15V is applied. Estimate the reverse saturation current at room temperature. (For Germanium, $\eta=1$)	[2]	1	3
Q.2(b) Explain the construction and working of center tap full wave rectifier with circuit diagram. Derive the rectification efficiency for it.	[3]	1	2,3
Q.3(a) Both Zener and Avalanche breakdown mechanisms are used in voltage regulation circuits. Evaluate the suitability of each mechanism for low-voltage and high-voltage applications.	[2]	1	5
Q.3(b) In the circuit shown below, $V=10V$, $R=1K\Omega$, and breakdown voltage of Zener diode is 6V. Determine I_z if (i) $R_L=100\Omega$ and (ii) $R_L=9K\Omega$	[3]	1	4

 

Q.4(a) Derive the relationship between the current gain coefficients α (common-base), β (common-emitter), and γ (common-collector) of a BJT.	[2]	2	3
Q.4(b) Draw the circuit diagrams of an NPN transistor in Common-Base (CB), Common-Collector (CC), and Common-Emitter (CE) configurations. Label all terminals, input and output.	[3]	2	2
Q.5(a) Draw and explain the fixed-bias circuit for an NPN transistor in common-emitter configuration. Using circuit analysis, derive the expressions for the zero-signal collector current and collector-to-emitter voltage (V_{CE}).	[2]	2	2,3
Q.5(b) Design a fixed bias circuit for a CE transistor amplifier such that the operating point is $V_{CE}=8V$ and $I_c=2mA$. The circuit is supplied with a fixed 15V DC supply and silicon transistor with $\beta=100$.	[3]	2	6