

**BIRLA INSTITUTE OF TECHNOLOGY, MESRA, RANCHI  
(END SEMESTER EXAMINATION)**

CLASS: BTECH  
BRANCH: EEE

SEMESTER: III<sup>rd</sup>/ADD  
SESSION: MO/2025

SUBJECT: EE24201 ELECTRICAL MEASUREMENT AND INSTRUMENTATION


TIME: 3 Hours

FULL MARKS: 50

**INSTRUCTIONS:**

1. The question paper contains 5 questions each of 10 marks and total 50 marks.
2. Attempt all questions.
3. The missing data, if any, may be assumed suitably.
4. Before attempting the question paper, be sure that you have got the correct question paper.
5. Tables/Data hand book/Graph paper etc. to be supplied to the candidates in the examination hall.

- |  | CO    | BL |
|--|-------|----|
| Q.1(a) Describe the basic blocks of a generalized Instrumentation System? Draw the various blocks and explain their functions.   | [5] 1 | 1  |
| Q.1(b) A 160pF capacitor, and inductor of 160μH and a resistor of 1200Ω are connected in series.   | [5] 1 | 6  |
| (a) If all the three components have ±0% error, compute the resonant frequency of the combination.   |       |    |
| (b) If all the three components have +10% errors compute the expected resonance frequency of the combination and the percentage error when compared to the result of part (a)  |       |    |
| (c) If all the three components are -10%, compute the expected resonant frequency and the percentage error when compared to the result of part (a).  |       |    |
| Q.2(a) Describe the constructional details and principle of operation of a d'Arsonval galvanometer. Derive the expression for steady state deflection.   | [5] 2 | 2  |
| Q.2(b) A moving coil ammeter has a fixed shunt of 0.02Ω. With a coil resistance of R = 1000Ω and a potential difference of 500mV across it, full scale deflection is obtained.   | [5] 2 | 3  |
| (a) To what shunted current does this correspond?  |       |    |
| (b) Calculate the value of R to give full scale deflection when shunted current I is 10A.  |       |    |
| (c) With what value of R is 40% deflection obtained with I = 100A?   |       |    |
| Q.3(a) The arms of a four arms bridge ABCD, supplied with sinusoidal voltage, have the following values:<br>Arm AB: A resistor of 200Ω in parallel with a capacitor 1μF.<br>Arm BC: 400Ω resistor; Arm CD: A 1000Ω resistor; Arm DA: A resistor of R <sub>2</sub> in series with a 2 μF capacitor.<br>Determine the value of R <sub>2</sub> and the frequency at which the bridge will balance.          | [5] 3 | 3  |
| Q.3(b) Describe the Varley loop test used for localization of cable faults. How is this method different from Murray loop test?  | [5] 3 | 2  |
| Q.4(a) Draw the block diagram of a general purpose CRO and explain the function of focus control and synchronization control.  | [5] 4 | 1  |
| Q.4(b) The sketches shown in figure below display Lissajous patterns for cases where voltages of same frequency but having phase difference are connected to Y and X plates of the oscilloscope. Find the phase difference in each case. The spot generating the patterns moves in a clockwise direction. Calculate the angles if the spot generating the patterns moves in the anticlockwise direction. | [5] 4 | 3  |

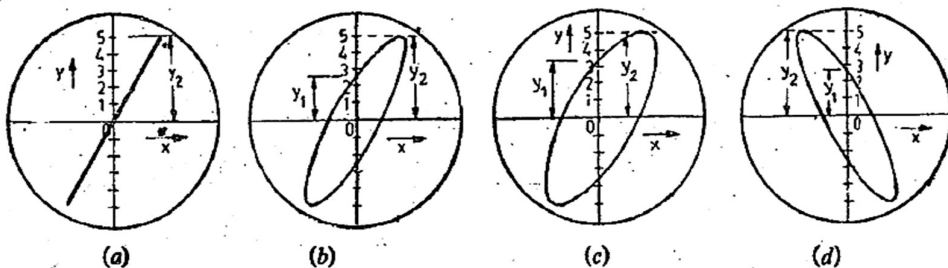

- Q.5(a) Differentiate between the following citing suitable examples: [5] 5 2  
(a) Active and passive transducers  
(b) Primary and Secondary transducers  
(c) Analog and digital transducers.
- Q.5(b) Describe the working principle of linear variable differential transformer. Why is the word “differential” used in Linear Variable Differential Transformer”? Why is it called as “Transformer”? [5] 5 2

.....19/11/2025.....E