

**BIRLA INSTITUTE OF TECHNOLOGY, MESRA, RANCHI
(END SEMESTER EXAMINATION)**

CLASS: B. TECH.
BRANCH: EEE

SEMESTER : III/ADD
SESSION : MO/2025

SUBJECT: EE24203 ANALOG AND DIGITAL CIRCUITS

TIME: 3 Hours


FULL MARKS: 50

INSTRUCTIONS:


1. The question paper contains 5 questions each of 10 marks and total 50 marks.
2. Attempt all questions.
3. The missing data, if any, may be assumed suitably.
4. Before attempting the question paper, be sure that you have got the correct question paper.
5. Tables/Data hand book/Graph paper etc. to be supplied to the candidates in the examination hall.

CO BL

 
Q.1(a) For the circuit shown below, assume that the zener diode is ideal with a breakdown voltage of 6 volts. Draw the waveform observed across R for sinusoidal input voltage. [5]



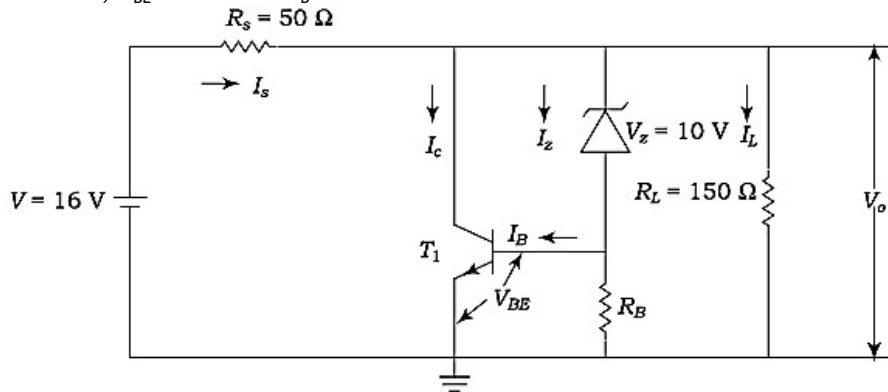Q.1(b) Write, with a suitable circuit diagram, the working principle of a positive clamper circuit. [5]
A transistor shunt regulated power supply is shown in Figure. Determine (a) the output voltage (V_O), (b) load current (I_L), and (c) source current (I_S). Assume zener resistance is equal to zero, $V_{BE} = 0.7 \text{ V}$ and $R_B = \infty$.



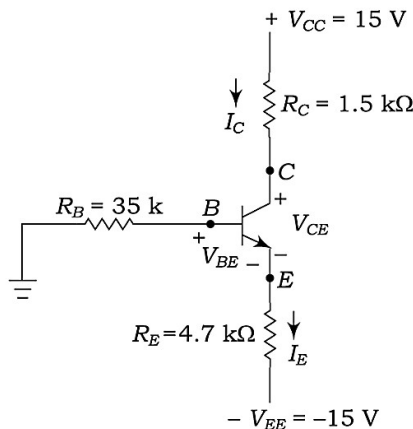Q.2(a) Determine the emitter current, collector current, and collector to emitter voltage. [5]
Assume $V_{BE} = 0.75 \text{ V}$ and $\beta = 70$.



PTO


Q.2(b) Draw the high-frequency small-signal hybrid- π model of a voltage-divider-biased CE amplifier and its complete frequency-response curve. [5]
 Illustrate the working of a Wien bridge oscillator with a neat circuit diagram.

Q.3(a) Determine the gain of a common-source amplifier with voltage-divider bias in the mid-band region. [5]

Q.3(b) Determine the radix r : $(BEE)_r = (2699)_{10}$ [5]
 Draw and explain the working principal of CMOS Inverter.


Q.4(a) $X = 01110$ and $Y = 11001$ are two 5-bit binary numbers represented in two's complement format. Find out the 6 bits sum of X and Y represented in two's complement format. [5]
 Optimize the following Boolean functions F together with the don't-care conditions d in sum-of-products $F(W, X, Y, Z) = \Sigma m(5, 6, 11, 12)$.

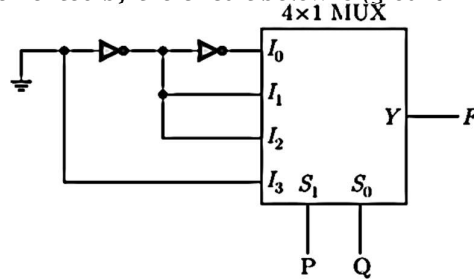Q.4(b) The logic function implemented by the circuit below is (ground implies a logic "0") [5]




With the help of logic diagram and truth table, design a full Adder and realize a full Adder using only NAND gates

 Q.5(a) In a J-K flip-flop we have $J = Q$ and $K = 1$. Assuming the flip flop was initially cleared and then clocked for 6 pulses, what is the sequence at the Q output? [5]



 Find out the maximum number of clock pulses the counter can count.



Q.5(b) Design a 3-bit serial in serial out shift register. [5]