

**BIRLA INSTITUTE OF TECHNOLOGY, MESRA, RANCHI
(END SEMESTER EXAMINATION)**

CLASS: BTECH
BRANCH: EEE

SEMESTER : III/ADD
SESSION : MO/2025

SUBJECT: EE24209 CIRCUIT THEORY

TIME: 3 Hours

FULL MARKS: 50

INSTRUCTIONS:

1. The question paper contains 5 questions each of 10 marks and total 50 marks.
2. Attempt all questions.
3. The missing data, if any, may be assumed suitably.
4. Before attempting the question paper, be sure that you have got the correct question paper.
5. Tables/Data handbook/Graph paper etc. to be supplied to the candidates in the examination hall.

Q.1(a) Analyze the graph of the network as in Fig. 1 and evaluate the possible trees. [2]

CO BL
CO1, BL3
CO2 BL4
&
CO4

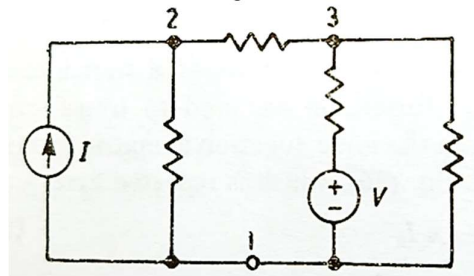


Fig.

Q.1(b) Select a suitable tree based on the obtained graph for Fig. 2 and determine the tie-set matrix. Analyze the KVL equation from the tie-set matrix. [3]

CO1, BL3
CO2 BL4
&
CO4

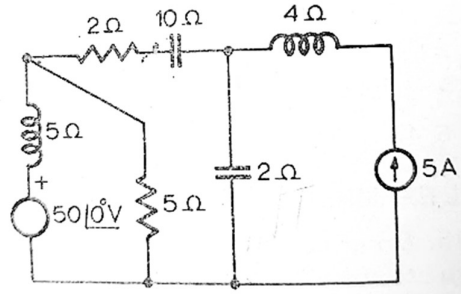


Fig. 2

Q.1(c) Analyze the graph for Fig. 3 as shown below. Select a suitable tree and obtain the (i) cut-set matrix and (ii) tie-set matrix. [5]

CO1, BL3
CO2 BL4
&
CO4

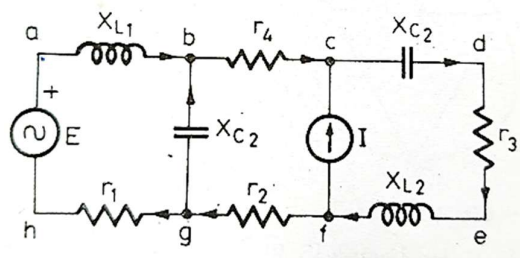


Fig. 3

- Q.2(a) Validate the Tellegen's Theorem for the network as in Fig. 4 with $V_1 = 10\text{ V}$, $V_2 = 4\text{ V}$, $V_4 = 6\text{ V}$, $I_1 = I_2 = 2\text{ A}$, $I_3 = 4\text{ A}$. [5] CO2 & BL1
CO4 BL4

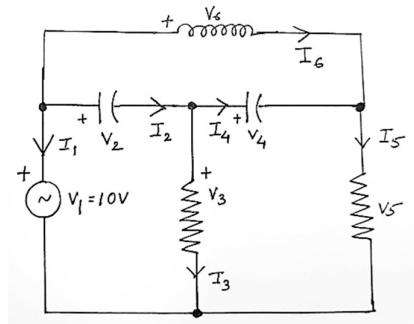


Fig. 4

- Q.2(b) Evaluate the voltage V_x in the network shown in Fig. 5 and verify the reciprocity theorem. [5] CO2 & BL1
CO4 BL4

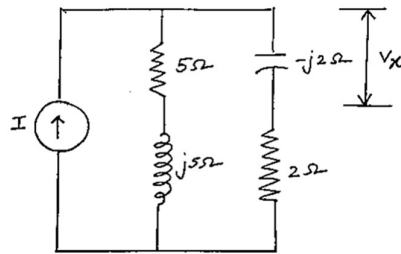


Fig. 5

- Q.3(a) Analyze the driving point admittance function and the respective pole-zero plot for the circuit as in Fig. 6. [5] CO1 & BL1
CO3 BL4

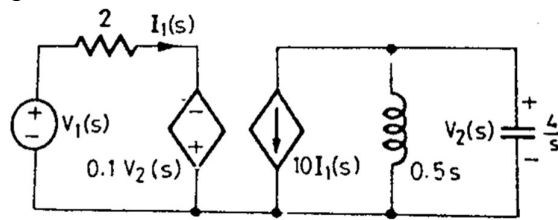


Fig. 6

- Q.3(b) The Z parameters of a circuit are given by $\begin{bmatrix} 4 & 1 \\ 3 & 3 \end{bmatrix}$, evaluate (i) transmission parameters and (ii) h-parameters. [5] CO1, CO2 & CO4 BL1 BL4

- Q.4(a) Test the positive realness of the function. [5] CO1, CO2 & CO4 BL1 BL4
- $$z(s) = \frac{s^3 + 5s^2 + 9s + 3}{s^3 + 4s^2 + 7s + 9}$$

- Q.4(b) Realize the following impedance function in both Cauer Form-I & Cauer Form-II and synthesize the corresponding networks. [5] CO1, CO2 & CO4 BL1 BL4
- $$z(s) = \frac{12s^4 + 10s^2 + 1}{3s^3 + 2s}$$

- Q.5(a) Considering RC series circuit with input voltage (V_i), analyze the type of filter when output voltage (V_o) is considered across (i) capacitor, (ii) resistor. [5] CO5 BL1 BL4

- Q.5(b) Analyze the second order low pass filter using Butterworth Approximation. [5] CO5 BL1 BL4