

**BIRLA INSTITUTE OF TECHNOLOGY, MESRA, RANCHI
(MID SEMESTER EXAMINATION)**

**CLASS: B.TECH
BRANCH: EEE**

**SEMESTER : V/ADD
SESSION : MO/2025**

SUBJECT: EE353 POWER ELECTRONICS

TIME: 02 Hours


FULL MARKS: 25

INSTRUCTIONS:

1. The question paper contains 5 questions each of 5 marks and total 25 marks.
2. Attempt all questions.
3. The missing data, if any, may be assumed suitably.
4. Tables/Data handbook/Graph paper etc., if applicable, will be supplied to the candidates

		CO	BL
Q.1(a) List various applications of power electronics.	[2]	1	1
Q.1(b) Explain the static $V-I$ and transfer characteristics of the IGBT with the help of a circuit diagram and suitable waveform.	[3]	1	2
Q.2(a) List the differences between Power MOSFET and IGBT.	[2]	1	1
Q.2(b) Explain the switching characteristics of power MOSFET with the help of a suitable waveform.	[3]	1	2
Q.3(a) Discuss any four anode voltage ratings for a thyristor.	[2]	2	2
Q.3(b) Explain the two-transistor model of a thyristor and describe how the anode current is related to the current gains of the two transistors.	[3]	2	2
Q.4(a) Explain di/dt and dv/dt protection of a thyristor.	[2]	2	3
Q.4(b) Thyristor shown in Fig.1 has I^2t rating of $20A^2s$. If terminal A gets short-circuited to ground, calculate the fault clearance time so that SCR is not damaged.	[3]	2	3

Fig. 1

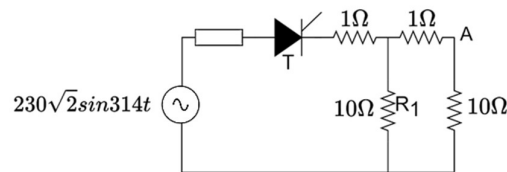

Q.5(a) Explain the term string efficiency and the derating factor.	[2]	2	2
Q.5(b) SCR with a rating of 2000 V and 400 A, are available to be used in a string to handle 12 kV and 2 kA. Calculate the number of series and parallel units required in case the derating factor is 0.4.	[3]	2	3