

**BIRLA INSTITUTE OF TECHNOLOGY, MESRA, RANCHI  
(END SEMESTER EXAMINATION)**

**CLASS: B.Tech.  
BRANCH: EEE**

**SEMESTER : VII  
SESSION : MO/2025**

**SUBJECT: EE507 ADVANCED POWER ELECTRONICS**

**TIME: 3 Hours**

**FULL MARKS: 50**

**INSTRUCTIONS:**

1. The question paper contains 5 questions each of 10 marks and total 50 marks.
  2. Attempt all questions.
  3. The missing data, if any, may be assumed suitably.
  4. Before attempting the question paper, be sure that you have got the correct question paper.
  5. Tables/Data hand book/Graph paper etc. to be supplied to the candidates in the examination hall.
- 

			CO	BL	Module No.
Q.1(a)	Explain the static and dynamic characteristics of an IGBT. Compare it with a Power MOSFET in terms of switching speed, loss, and drive requirements.	[5]	CO1	BL2, BL3	I
Q.1(b)	Draw and explain a suitable gate driver circuit for MOSFET with protection features.	[5]	CO1	BL3	I
Q.2(a)	Explain the operation of a forward converter with circuit diagram and waveforms.	[5]	CO2	BL2	II
Q.2(b)	Differentiate between Flyback and Forward converters. Discuss their applications in SMPS design.	[5]	CO2	BL2- BL4	II
Q.3(a)	Explain the concept of Space Vector PWM and its advantages over sinusoidal PWM.	[5]	CO2	BL3	III
Q.3(b)	Describe the operating principle and advantages of a cascaded H-Bridge multilevel inverter.	[5]	CO3	BL3	III
Q.4(a)	With neat diagram and waveforms, explain the operation of a Zero Voltage Switching (ZVS) resonant converter. [5]	[5]	CO3	BL4	IV
Q.4(b)	A series resonant inverter has $L = 40 \mu\text{H}$ , $C = 8 \mu\text{F}$ , and load resistance $R = 3 \Omega$ . Determine: (i) Resonant frequency, (ii) RMS current through the load, (iii) Quality factor Q.	[5]	CO2	BL3	IV
Q.5(a)	Draw and explain the internal functional block diagram of UC3825 IC.	[5]	CO1, CO5	BL2	V
Q.5(b)	Write short notes on Intelligent Power Module (IPM) and its role in industrial drives.	[5]	CO5	BL3, BL5	V

:::24/11/2025:::M