

**BIRLA INSTITUTE OF TECHNOLOGY, MESRA, RANCHI
(END SEMESTER EXAMINATION)**

**CLASS: B.TECH/IMSC
BRANCH: BT/CIVIL/CEP&P/CHEM. ENGG./MECH/PROD/FT/PHYSICS**

**SEMESTER : II
SESSION : SP/19**


**SUBJECT: EC101 BASICS OF ELECTRONICS AND COMMUNICATION ENGINEERING
TIME: 3.00 Hrs.**

FULL MARKS: 50

INSTRUCTIONS:

1. The question paper contains 5 questions each of 10 marks and total 50 marks.
 2. Attempt all questions.
 3. The missing data, if any, may be assumed suitably.
 4. Before attempting the question paper, be sure that you have got the correct question paper.
 5. Tables/Data hand book/Graph paper etc. to be supplied to the candidates in the examination hall.
-

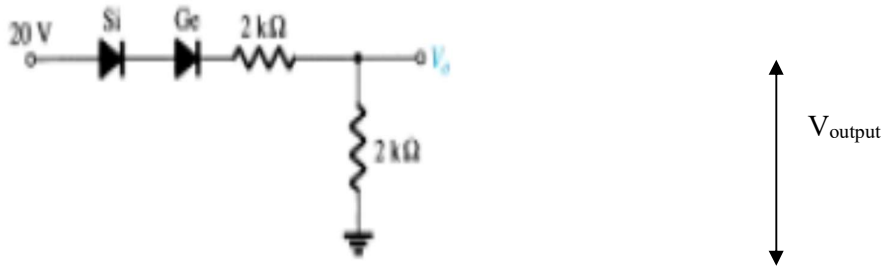- Q.1(a) Define donor and acceptor impurities. Also, derive the expression for diode dynamic resistance. [5]
Q.1(b) Explain the transition and diffusion capacitance of the p-n junction diode. Determine the output voltage and current through the following circuit. [5]



- Q.2(a) Elaborate the emitter-bias configuration with suitable example. How collector feedback configuration will improve the stability? Explain with a suitable example. [5]
Q.2(b) Outline the advantages of the FET over conventional BJT. Draw the JFET & MOSFET symbols for n-channel and p-channel. [5]
- Q.3(a) What is Barkhausen criterion? How does Hartley oscillator differ from Colpitt's oscillator in construction? [5]
Q.3(b) What do you mean by CMRR and slew rate? Determine the output voltage of an OP-AMP for input voltages of $V_1 = 150\mu\text{V}$ and $V_2 = 140\mu\text{V}$. The amplifier has a differential gain of $A_d = 4000$ and the value of CMRR is 100. [5]
- Q.4(a) Simplify the Boolean expression $N = (A + A'B + C'D + C)$ and prove that $N = (A + B + C + D)$. Also realize its output using NOR gates. [5]
Q.4(b) Construct a half-subtractor circuit and express the following function in a sum of minterms $F(w,x,y,z) = wxy' + y'z + wxz' + w'x'z$ [5]
- Q.5(a) Draw the block diagram of a communication system and briefly explain. Also define modulation index of an amplitude modulated signal. [5]
Q.5(b) The tuned circuit of an oscillator in a simple AM transmitter employs a $50\mu\text{H}$ coil and 2 nF capacitor. If the oscillator output is modulated by audio frequencies up to 10 kHz , estimate the frequency range occupied by the sideband. [5]