BIRLA INSTITUTE OF TECHNOLOGY, MESRA, RANCHI (END SEMESTER EXAMINATION)

(END SEMESTER EXAMINATION)			
CLASS: BRANCH:	M. Tech ECE	SEMESTER : II SESSION : SP/19	•
TIME:	SUBJECT: EC570 EMBEDDED SYSTEM DESIGN 3 Hours	FULL MARKS: 5	0
 INSTRUCTIONS: 1. The question paper contains 5 questions each of 10 marks and total 50 marks. 2. Attempt all questions. 3. The missing data, if any, may be assumed suitably. 4. Before attempting the question paper, be sure that you have got the correct question paper. 5. Tables/Data hand book/Graph paper etc. to be supplied to the candidates in the examination hall. 			
Q.1(a)	Discuss the various common characteristics of a real-time embedded system. them.	Briefly explain	[5]
Q.1(b)	Paraphrase "hardware-software co-design" with respect to embedded system.		[5]
Q.2(a)	Write the name of at least 15 special function registers (SFRs), which are embedded in microcontroller 8051.		[5]
Q.2(b)			[5]
Q.3(a)	Diagram a buzzer driver circuit in such a way that the buzzer is 'ON' when a high pulse is sent from FPGA and briefly explain it.		[5]
Q.3(b)	Diagram an Optical Sensor Interfacing (with Infrared sensor) circuit for measuring rotating disc. Analyse and explain the same.	g the speed of a	[5]
Q.4(a)	Schematize the sensor interfacing and data processing setup. Evaluate and appra of its constituents.	aise significance	[5]
Q.4(b)	Design a 3-bit PRSG (pseudo random sequence generator) with non-zero seed t tabulate the generated test pattern. Evaluate and appraise its significance.	est pattern and	[5]
Q.5(a)	What are the issues of interfacing DC motor directly with microprocessor, micro FPGA? Design a DC motor interfacing circuit, which may solve the issues.	ocontroller, and	[5]
Q.5(b)	Assume that one DC motor is configured with a control system through a motor Design and develop a digital system to operate the motor in the clockwise and directions and stop it for the predetermined period.		[5]

:::::24/04/2019 M:::::