

**BIRLA INSTITUTE OF TECHNOLOGY, MESRA, RANCHI
(MID SEMESTER EXAMINATION)**

CLASS: BE/IMSC
BRANCH: BT/CHEMICAL/CP&P/CIVIL/MECH/PROD/FT/PHYSICS

SEMESTER: II
SESSION: SP/2020

SUBJECT: EC101 BASIC ELECTRONICS & COMMUNICATION ENGINEERING

TIME: 2 HOURS

FULL MARKS: 25

INSTRUCTIONS:

1. The total marks of the questions are 25.
2. Candidates may attempt for all 25 marks.
3. Before attempting the question paper, be sure that you have got the correct question paper.
4. The missing data, if any, may be assumed suitably.
5. Tables/Data hand book/Graph paper etc. to be supplied to the candidates in the examination hall.

- | | | | CO | BL |
|----|---|-----|-----|-------|
| Q1 | (a) Explain the Intrinsic & Extrinsic Semiconductor with suitable examples. | [2] | CO1 | L2 |
| Q1 | (b) An abrupt <i>pn</i> junction in silicon has doping densities $N_A = 10^{18}$ atoms/cm ³ and $N_D = 10^{19}$ /cm ³ atoms/cm ³ . Calculate the junction built-in potential Ψ_0 with intrinsic concentration of $n_i = 1.5 \times 10^{10}$ atoms/cm ³ . | [3] | CO1 | L3 |
| Q2 | (a) An abrupt <i>pn</i> junction in silicon has doping densities $N_A = 10^{15}$ atoms/cm ³ and $N_D = 10^{16}$ atoms/cm ³ . Calculate the reverse bias voltage at depletion-layer depths (penetration in p-side) is 3.5μ and junction built-in potential $\Psi_0 = 638$ mV at 300°K. | [2] | CO1 | L3 |
| Q2 | (b) Demonstrate the charge density, electric field and electrostatic potential with suitable energy diagram if abrupt PN junction in reverse bias. Show the use of diode if operate in avalanche region. | [3] | CO1 | L3 |
| Q3 | (a) Demonstrate the half wave and full wave rectifier and evaluate the DC voltage and current. Explain the need of filter after first stage of full wave rectifier. | [2] | CO1 | L3&L2 |
| Q3 | (b) In Figure1, the Zener voltage is 15V, the knee current is negligible and the Zener resistance is 30Ω. If the input voltage (V_i) ranges from 40V to 50V, then calculate output voltage (V_{out}) ranges. | [3] | CO1 | L3 |

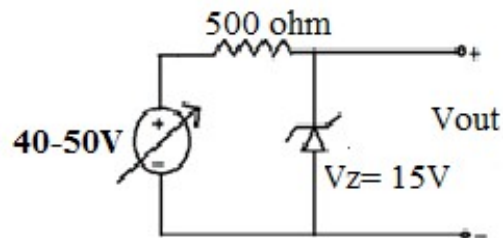


Fig.1.

- | | | | | | |
|----|-----|---|-----|-----|-------|
| Q4 | (a) | Explain the working region of BJT. Show the relation between α , β , and γ in common base, common emitter and common collector configuration. | [2] | CO2 | L2&L3 |
|----|-----|---|-----|-----|-------|

- Q4 (b) From Figure2 calculate the base current I_B , collector current I_C and collector base voltage V_{CB} . [3] CO2 L3

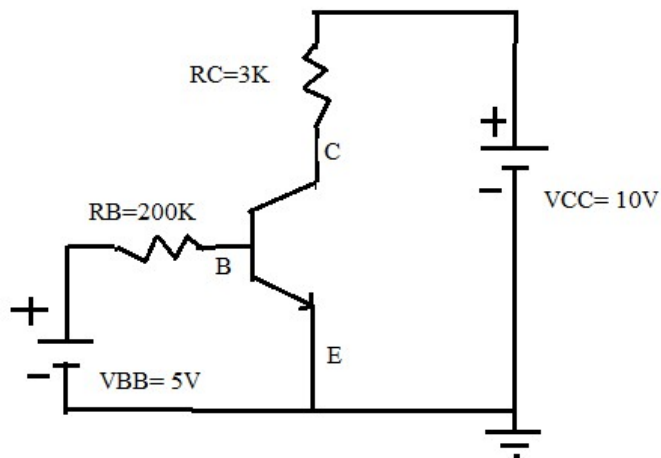


Fig.2

- Q5 (a) Show the structure of JFET, channel formation, pinch Off and saturation voltage characteristics. [2] CO2 L2
- Q5 (b) Prepare the fabrication view of NMOS transistor and also draw the I_{DS} (drain to source current)- V_{DS} (drain to source voltage) characteristics and explain the working region of transistors. [3] CO2 L2

:::: 28/02/2020M ::::