

**BIRLA INSTITUTE OF TECHNOLOGY, MESRA, RANCHI**  
(END SEMESTER EXAMINATION)

CLASS: BTECH/IMSC  
BRANCH: BT/CHEMICAL/CIVIL/MECH/PROD/FT

SEMESTER : II  
SESSION : SP/2022


SUBJECT: EC101 BASICS OF ELECTRONICS AND COMMUNICATION ENGINEERING  
TIME: 3 HOURS

FULL MARKS: 50


**INSTRUCTIONS:**

1. The question paper contains 5 questions each of 10 marks and total 50 marks.
2. Attempt all questions.
3. The missing data, if any, may be assumed suitably.
4. Tables/Data hand book/Graph paper etc. to be supplied to the candidates in the examination hall.

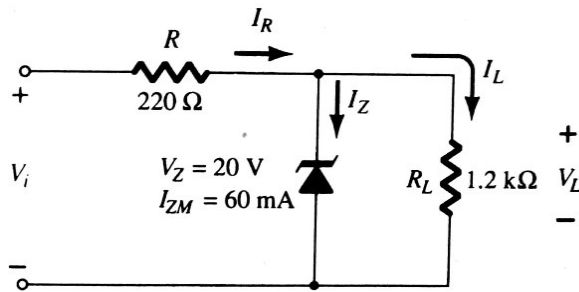- Q.1(a) Explain the working principle of a full-wave rectifier with a C-type filter and resistive load. Draw the related waveforms and derive the expression for the ripple factor. [5]
- Q.1(b) Determine the range of values of  $V_i$  that will maintain the Zener diode of the following figure in the "on" state. [5]



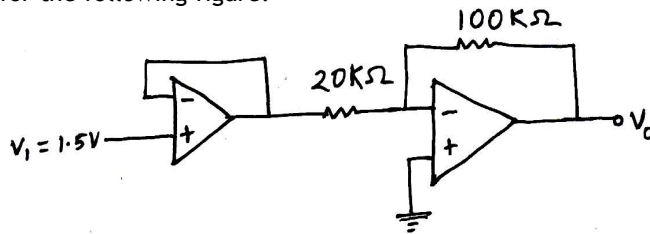- Q.2(a) What is the need for biasing? Draw the fixed bias circuit and derive the expression for  $V_{CE}$  and  $I_C$ . [1+4]
- Q.2(b) Compare the Depletion type MOSFET and Enhancement type MOSFET. Find the value for drain current of a JFET with  $I_{DSS} = 12\text{mA}$ ,  $V_P = -6\text{V}$  and  $V_{GS} = -3\text{V}$ . [5]
- Q.3(a) List out any four advantages of negative feedback. An amplifier with negative feedback gives an output of 12.5 V with an input of 1.5 V. When feedback is removed, it requires 0.25 V input for the same output. Find the voltage gain without feedback ( $A$ ), and the value of feedback factor ( $\beta$ ). [2+3]
- Q.3(b) Write the characteristics of an ideal operational amplifier. Find the value of the output voltage  $V_0$  for the following figure. [5]



- Q.4(a) Implement the function  $F(A, B, C, D) = A + \overline{BC} + AB\overline{D} + ABCD$  with basic logic-gates [5]
- Q.4(b) Implement a full adder circuit by using a minimum number of two inputs NAND gates [5]
- Q.5(a) Explain the different elements of an electronics communication system with a neat block diagram. Determine the required minimum antenna height for transmitting a voice signal of 1 KHz. [5]
- Q.5(b) What do you mean by modulation and demodulation? Why is modulation required in communication system? Explain the Amplitude modulation briefly. [5]