



Name: Roll No.:


Branch: Signature of Invigilator:

Semester: VIth Date: 29/04/2022 (MORNING)

Subject with Code: EE355 POWER SYSTEM ANALYSIS


Marks Obtained	Section A (30)	Section B (20)	Total Marks (50)

INSTRUCTION TO CANDIDATE

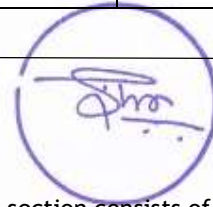


1. The booklet (question paper cum answer sheet) consists of two sections. First section consists of MCQs of 30 marks. Candidates may mark the correct answer in the space provided / may also write answers in the answer sheet provided. The Second section of question paper consists of subjective questions of 20 marks. The candidates may write the answers for these questions in the answer sheets provided with the question booklet.
2. The booklet will be distributed to the candidates before 05 minutes of the examination. Candidates should write their roll no. in each page of the booklet.
3. Place the Student ID card, Registration Slip and No Dues Clearance (if applicable) on your desk. All the entries on the cover page must be filled at the specified space.
4. Carrying or using of mobile phone / any electronic gadgets (except regular scientific calculator)/chits are strictly prohibited inside the examination hall as it comes under the category of unfair means.
5. No candidate should be allowed to enter the examination hall later than 10 minutes after the commencement of examination. Candidates are not allowed to go out of the examination hall/room during the first 30 minutes and last 10 minutes of the examination.
6. Write on both side of the leaf and use pens with same ink.
7. The medium of examination is English. Answer book written in language other than English is liable to be rejected.
8. All attached sheets such as graph papers, drawing sheets etc. should be properly folded to the size of the answer book and tagged with the answer book by the candidate at least 05 minutes before the end of examination.
9. The door of examination hall will be closed 10 minutes before the end of examination. Do not leave the examination hall until the invigilators instruct you to do so.
10. Always maintain the highest level of integrity. Remember you are a BITian.
11. Candidates need to submit the question paper cum answer sheets before leaving the examination hall.


a)

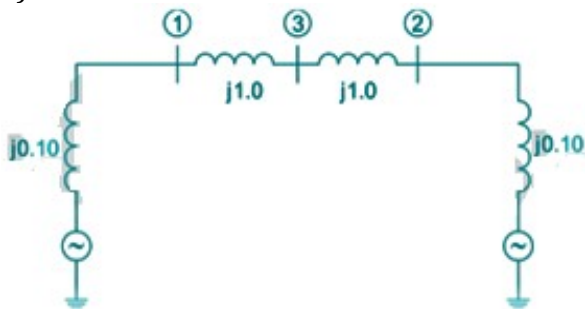


b)

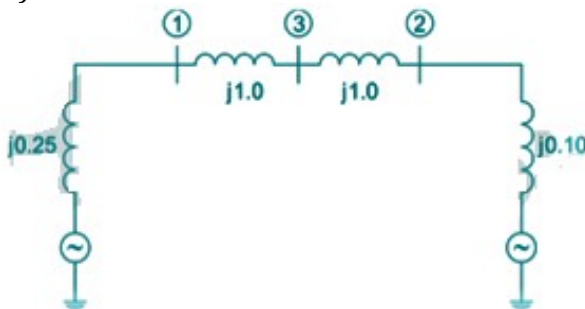

c)

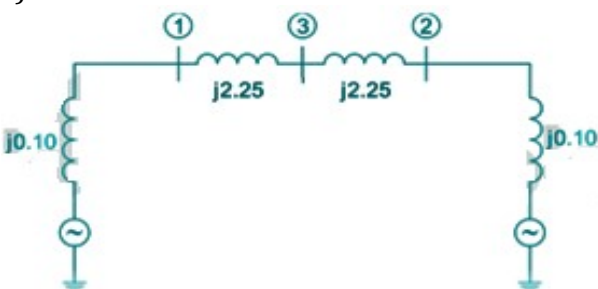

d)

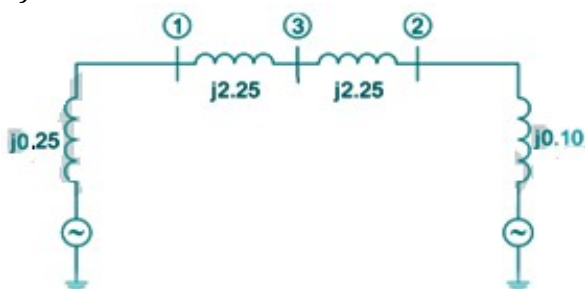


Q4

A new generator having $E_g = 1.4 \angle 30$ pu [equivalent to $(1.212 + j 0.70)$ pu] and synchronous reactance ' X_s ' of 1.0 pu on the system base, is to be connected to a bus having voltage V_t in the existing power system. This existing power system can be represented by Thevenin's voltage $E_{th} = 0.9 \angle 0$ pu in series with


2


	<p> a) $1.310\angle-107^\circ$ A b) $0.332\angle-120^\circ$ A c) $0.996\angle-120^\circ$ A d) $3.510\angle-81^\circ$ A </p>	
Q15	<p>The severity of line-to-ground and three phase faults at the terminals of an unloaded synchronous generator is to be same. If the terminal voltage is 1.0 p.u. and $Z_1=Z_2=j0.1$ p.u., $Z_0=j0.05$ p.u., for the alternator, then the required inductive reactance for neutral grounding is</p> <p> a) 0.0166 pu b) 0.05 pu c) 0.1 pu d) 0.15 pu </p>	1
Q16	<p>Which among the following reactance have a greater value?</p> <p> a) Sub transient reactance b) Transient reactance c) Synchronous reactance d) None of these </p>	1
Q17	<p>Why are series reactors used?</p> <p> a) Improve the transmission efficiency b) Improve the power factor of the power system c) To bring down the fault level within the capacity of switchgear instruments d) All of these </p>	1
Q18	<p>In which of the following given faults, all the sequence voltages at the fault point in a power system are equal?</p> <p> a) LG b) LLG c) LLL d) LL </p>	1
Q19	<p>The zero sequence current of a generator for line to ground fault is $j3$ pu. Then the current through the neutral during the fault is</p> <p> a) $j3$ b) $j1$ c) $j9$ d) $j6$ </p>	1
Q20	<p>Equal area criterion is employed to determine</p> <p> a) Steady State Stability b) Transient Stability c) Reactive Power Limit d) Rating of CB </p>	1

Q21	In rotor angle stability, condition for stability is a) $dP/d\delta = 0$ c) $dV/dt = 0$ b) $d\delta/dt = 0$ d) $dQ/d\delta = 0$	1
-----	---	---

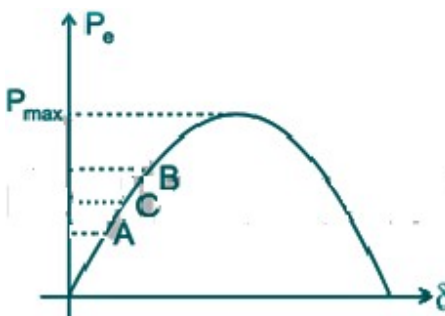Q22	During a disturbance on the synchronous machine, the rotor swing from A to B before finally settling down to a steady state at point C on the power angle curve. The speed of the machine during oscillation is synchronous at points  a) A and B c) B and C b) A and C d) only at C	1
-----	--	---

Section B

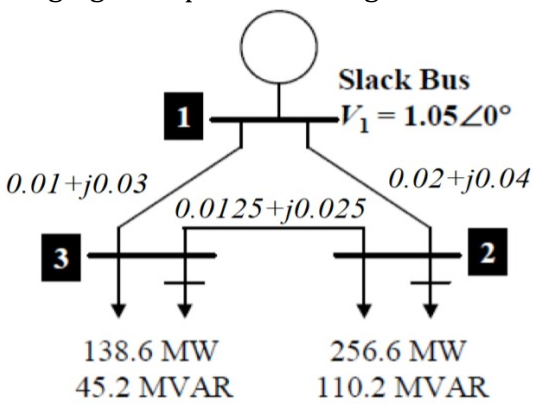Q23	Figure below shows the single-line diagram of three-bus power system with generation at bus 1. The scheduled loads at buses 2 and 3 are as marked on the diagram. Line impedances are marked in per unit on 100 MVA base and the line charging susceptance are neglected.  a) Using Gauss-Seidel method, determine the phasor values of the voltage at load buses 2 and 3 (P-Q buses). Perform the calculation for one iteration. b) Find slack bus real and reactive power. <p style="text-align: center;">Or</p>	4
-----	---	---

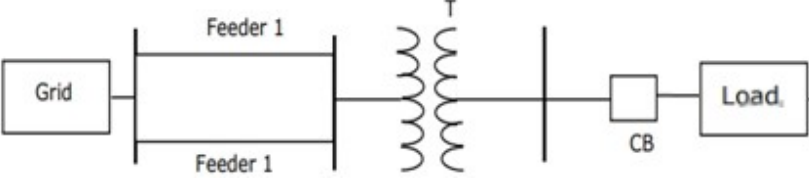	Explain the Newton Raphson load flow method for solution of basic power flow equations.	
Q24	<p>For the Y-bus matrix given in per unit values, where the first, second, third and fourth row refers to bus 1,2,3 and 4 respectively, draw the reactance diagram.</p> $Y_{bus} = j \begin{bmatrix} -6 & 2 & 2.5 & 0 \\ 2 & -10 & 2.5 & 4 \\ 2.5 & 2.5 & -9 & 4 \\ 0 & 4 & 4 & -8 \end{bmatrix}$	4
Q25	<p>A single line-to-ground fault occurs on an unloaded generator in phase a. The positive, negative, and zero sequence impedances of the generator are $j0.25$ p.u., $j0.25$ p.u., and $j0.15$ p.u. respectively. The generator neutral is grounded through a reactance of $j0.05$ p.u. The prefault generator terminal voltage is 1.0 p.u.</p> <p>(a) Draw the positive, negative, and zero sequence networks for the fault given. (b) Draw the interconnection of the sequence networks for the fault analysis. (c) Determine the fault current. (d) Determine the rating of the CB at a bus near the fault point.</p>	4
Q26	<p>Determine the required MVA rating of the circuit breaker CB for the system shown in given figure. Consider the grid as infinite bus. Choose 6 MVA as base. Transformer: 3-phase, 33/11 kV, 6 MVA, $0.01+j0.08$ p.u. impedance. Load: 3-phase 11 kV, 5800 kVA, 0.8 lag, $j0.2$ p.u. impedance. Impedance of each feeder $9+j18 \Omega$.</p>  <p style="text-align: center;">Or</p> <p>Draw a general circuit which can be used to determine the zero sequence network of two winding transformer. Using this circuit, draw the zero sequence networks of a) star-star transformer with star grounded on secondary side, b) delta-delta transformer, and c) delta-star transformer with star grounded with some neutral impedance Z_n.</p>	4
Q27	<p>Derive the swing equation of a synchronous machine swinging against an infinite bus. Clearly state the assumption in deducing the swing equation.</p> <p style="text-align: center;">Or</p>	4

	Why do we decide the rating of a circuit breaker on the basis of symmetrical short-circuit currents? Can feeder reactors permit the use of circuit breakers of lower ratings? Illustrate with example.	
--	--	--



BIRLA INSTITUTE OF TECHNOLOGY
MESRA - 835215, RANCHI, INDIA

Roll No.:





BIRLA INSTITUTE OF TECHNOLOGY
MESRA - 835215, RANCHI, INDIA

Roll No.:





BIRLA INSTITUTE OF TECHNOLOGY
MESRA - 835215, RANCHI, INDIA

Roll No.:





BIRLA INSTITUTE OF TECHNOLOGY
MESRA - 835215, RANCHI, INDIA

Roll No.:

