

BIRLA INSTITUTE OF TECHNOLOGY, MESRA, RANCHI
(END SEMESTER EXAMINATION)

CLASS:M.Tech
BRANCH:EEE

SEMESTER :2nd
SESSION : SP/22

SUBJECT: EE561 Embedded Control of Switching Power Converter

TIME: 2Hrs

FULL MARKS: 50

INSTRUCTIONS:

1. The question paper contains 5 questions each of 10 marks and total 50 marks.
 2. Attempt all questions.
 3. The missing data, if any, may be assumed suitably.
 4. Before attempting the question paper, be sure that you have got the correct question paper.
 5. Tables/Data hand book/Graph paper etc. to be supplied to the candidates in the examination hall.
-

- Q.1(a) Differentiate between linear power supply and switched mode power supply (SMPS) based upon operating point. [5]
CO1
- Q.1(b) List two application of SMPS in renewable energy harnessing. [5]
CO1
- Q.2(a) Obtain small signal model of a Boost converter. [5]
CO2
- Q.2(b) Obtain transfer functions relationship between small signal change in output voltage (\hat{V}_C) and small signal change input duty cycle (\hat{d}) in case of Boost Converter. [5]
CO2
- Q.3(a) Obtain transfer functions relationship between small signal change in inductor current (\hat{i}_L) signal change input duty cycle (\hat{d}) in case of Buck Converter. [5]
CO3
- Q.3(b) Obtain transfer functions relationship between small signal change in inductor current (\hat{i}_L) signal change input voltage (\hat{V}_g) in case of Buck Converter. [5]
CO3
- Q.4(a) Obtain input output current relationship of a Buck converter with at least one series non-ideality. [5]
CO4
- Q.4(b) Compare input-output relationship of current of non-ideal buck converter and ideal buck converter [5]
CO4
- Q.5(a) Write a program for ATMEGA2560 microcontroller to produce one pulse of 10kHz with 50% duty cycle in same phase using TIMER1. [5]
CO5
- Q.5(b) Design an embedded system block diagram for closed loop voltage control of DC-DC Buck converter [5]
CO5

29/04/2022 E