

BIRLA INSTITUTE OF TECHNOLOGY, MESRA, RANCHI
(MID SEMESTER EXAMINATION SP/2025)

CLASS: BCA
BRANCH: BCA

SEMESTER : II
SESSION : SP/2025

SUBJECT: CN123 BASICS OF DIGITAL COMPUTER AND LOGIC DESIGN

TIME: 02 Hours

FULL MARKS: 25

INSTRUCTIONS:

1. The question paper contains 5 questions each of 5 marks and total 25 marks.
 2. Attempt all questions.
 3. The missing data, if any, may be assumed suitably.
 4. Tables/Data handbook/Graph paper etc., if applicable, will be supplied to the candidates
-

		CO	BL
Q.1(a)	What do mean by digital computer? Explain it with suitable diagram.	[2]	1 1
Q.1(b)	Convert the following numbers from the given base to the bases indicated:	[3]	1 5
	(i) decimal 125.125 to binary, octal, and hexadecimal.		
	(ii) binary 1101010.001 to decimal, octal, hexadecimal.		
	(iii) Hexadecimal 2AC5.D to decimal, octal, and binary.		
Q.2(a)	Explain all the digital gates with their graphical symbol, algebraic function and also truth table.	[2]	1 1
Q.2(b)	Simplify the following Boolean functions to a minimum number of literals.	[3]	2 3
	(i) $xy + x'z + yz$ (ii) $xy + xz + yz'$		
Q.3(a)	What is K-map. How do you construct a K-Map for a given Boolean function of 4 variables?	[2]	3 1
Q.3(b)	Simplify the Boolean function: $F(A, B, C) = \sum(0, 2, 4, 5, 6)$ and design a circuit diagram for the simplified function.	[3]	3 3
Q.4(a)	Obtain the simplified expression in sum of product for following Boolean function using k-map.	[2]	3 5
	$ABD + A'C'D' + A'B + A'CD' + AB'D'$		
Q.4(b)	Simplify the Boolean function F together with the don't care conditions d in	[3]	3 5
	(i) sun-of-product form and (ii) product-of-sum form		
	$F(w, x, y, z) = \sum(0, 1, 3, 7, 8, 10)$ $d(w, x, y, z) = \sum(5, 6, 11, 15)$		
Q.5(a)	Define Combinational circuit with block diagram.	[2]	1 1
Q.5(b)	Design a full adder combinational circuit with two half adder circuit and an OR gate.	[3]	4 4

:25/02/2025:M