

BIRLA INSTITUTE OF TECHNOLOGY, MESRA, RANCHI  
(END SEMESTER EXAMINATION)

CLASS: I.M.Sc.  
BRANCH: PHYSICS

SEMESTER : IV  
SESSION : SP/2025

SUBJECT: SEC407 BASIC INSTRUMENTATION SKILLS

TIME: 3 Hours

FULL MARKS: 50

INSTRUCTIONS:

1. The question paper contains 5 questions each of 10 marks and total 50 marks.
  2. Attempt all questions.
  3. The missing data, if any, may be assumed suitably.
  4. Before attempting the question paper, be sure that you have got the correct question paper.
  5. Tables/Data hand book/Graph paper etc. to be supplied to the candidates in the examination hall.
- 

		CO	BL
Q.1(a)	List three techniques of voltage measurement. Explain any one of these in detail.	[5]	1 2
Q.1(b)	Explain how a galvanometer can be converted into (i) a voltmeter and (ii) an ammeter. The <i>internal resistance</i> and <i>full scale deflection current</i> of a moving coil galvanometer are $200\ \Omega$ and $100\ \mu A$ , respectively. Determine the resistance required to convert the galvanometer into an ammeter having a range of 10 mA.	[5]	1 3
Q.2(a)	Explain how a cathode ray oscilloscope (CRO) displays two traces simultaneously. Compare the <i>Alt</i> and <i>Chop</i> modes of displaying dual trace.	[5]	2 2
Q.2(b)	Discuss the advantages of digital storage oscilloscope (DSO) over a CRO.	[5]	2 2
Q.3(a)	What is the difference between a signal generator and a function generator? Describe the specifications of a typical function generator.	[5]	3 2
Q.3(b)	Define total harmonic distortion (THD) of a signal. Explain how THD can be measured using a DSO.	[5]	3 3
Q.4(a)	Explain the working of a Maxwell inductance bridge and obtain its balance conditions.	[5]	4 2
Q.4(b)	A strain gauge has a resistance of 350 ohms under no load condition and the resistance increases when the gauge is loaded. Design a Wheatstone bridge circuit such the bridge output is zero under no load condition and goes positive when loaded. The maximum current allowed through the strain gauge is 10 mA.	[5]	4 4
Q.5(a)	Sketch the block diagram of a digital multimeter and explain the function of each part.	[5]	5 2
Q.5(b)	Explain the technique of measuring the frequency of a signal accurately.	[5]	5 3

:::::01/05/2025 M:::::